

AC circuit



Agenda Today

1. Self-Inductance and Multi Inductance
2. Energy stored in Magnetic Field
3. RL Circuit
4. AC Circuit

Self-inductance(自感系数)

$$L = \Psi / I$$

Unit: H

According to Faraday's Law:

$$\varepsilon_L = -\frac{d\Psi}{dt} = -\frac{d(LI)}{dt} = -L\frac{dI}{dt}$$

Self-inductance of ideal solenoid


Cross section area : A

length: l

current : I

number of turns: N

permeability: μ

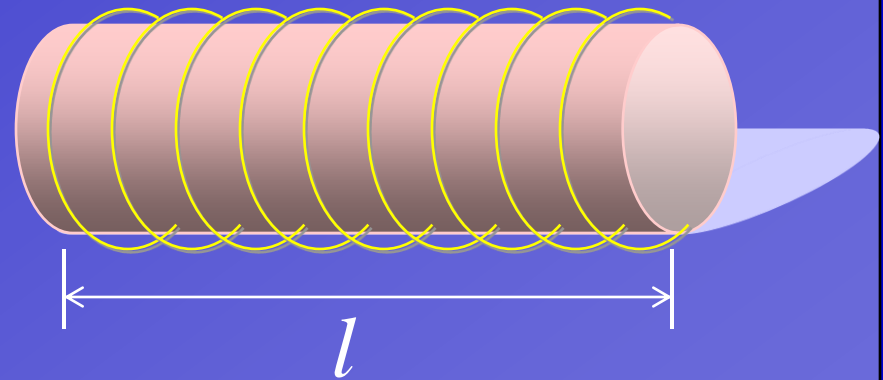

$$B = \mu \frac{N}{l} I$$


$$\Psi = NBS = \mu \frac{N^2}{l} IS$$

$$L = \frac{\Psi}{I} = \mu \frac{N^2}{l} S = \mu n^2 V$$
 Where n is turns per unit length

Multi induction (互感)

Emf caused by the change in current carried by another loop.

Multi inductance (互感系数)

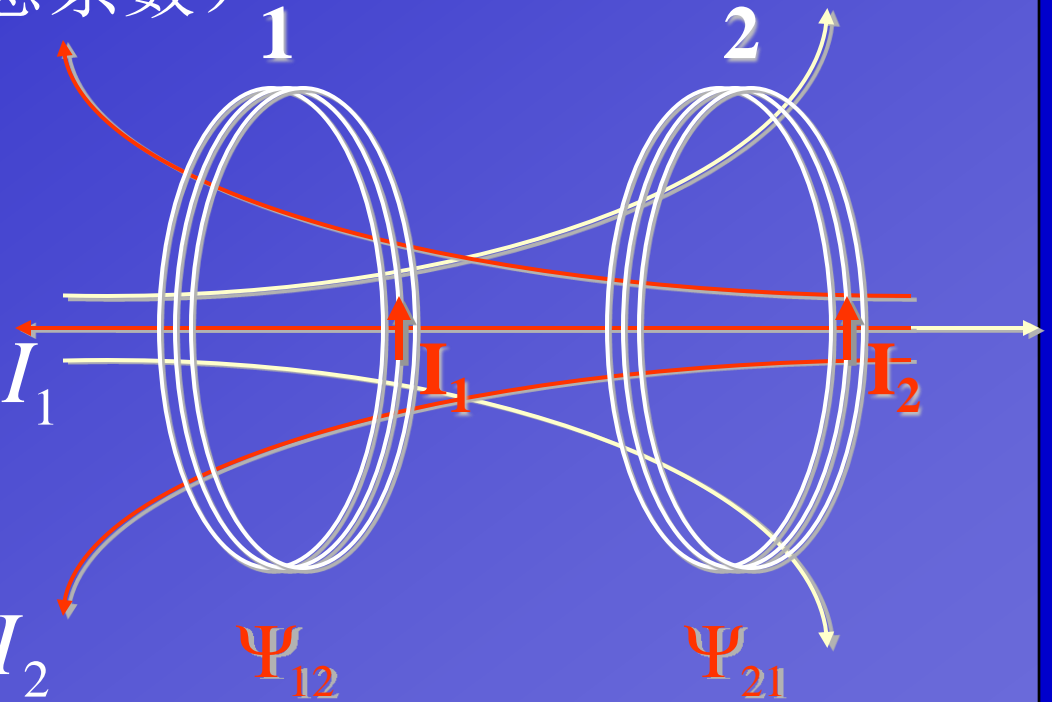

$$\Psi_{21} = N_2 \Phi_{21} = M_{21} I_1$$

$$\Psi_{12} = N_1 \Phi_{12} = M_{12} I_2$$


$$M_{12} = M_{21} = M$$

$$\begin{aligned} \mathcal{E}_{21} &= -M \frac{dI_1}{dt} \\ \mathcal{E}_{12} &= -M \frac{dI_2}{dt} \end{aligned}$$

互感概念演示仪



Tesla coil

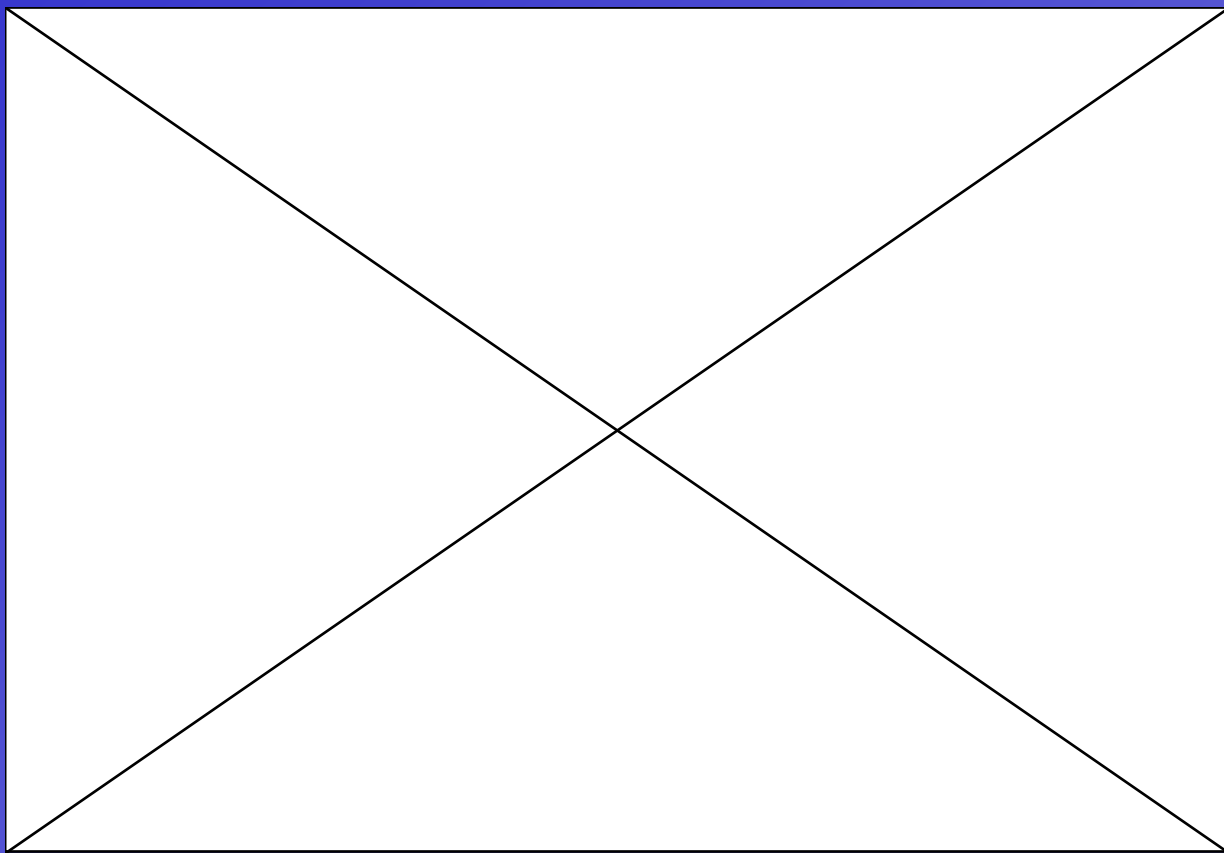


Example: Inside the magnetic material with permeability μ is a straight long wire and rectangular loop as the figure shows. find the multi inductance

solution

$$B = \frac{\mu_o I}{2\pi r}$$

$$d\Phi = BdS = \frac{\mu_o I}{2\pi r} l dr$$
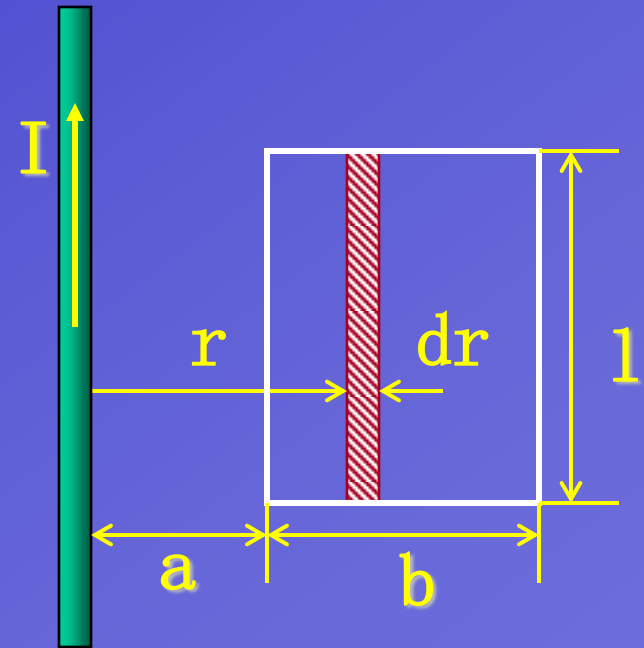
$$\Phi = \int_a^{a+b} \frac{\mu_o I l}{2\pi r} dr = \frac{\mu_o I l}{2\pi} \ln \frac{a+b}{a}$$



$$M = \frac{\Phi}{I} = \frac{\mu_o l}{2\pi} \ln \frac{a+b}{a}$$

RL circuit

By loop's rule:


$$\varepsilon - IR - L \frac{dI}{dt} = 0$$

$$I \Big|_{t=0} = 0$$

$$I \Big|_{t=\infty} = \frac{\varepsilon}{R}$$

$$I = \frac{\varepsilon}{R} \left(1 - e^{-\frac{t}{\tau}} \right)$$

where $\tau = \frac{L}{R}$

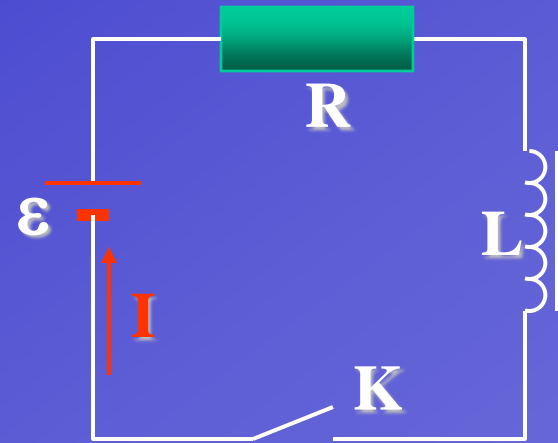

Energy stored in inductor

$$dE = UI dt = LI di$$

$$E = \int dE = \int_0^i LI di = \frac{1}{2} LI^2$$

Energy stored in multi inductors

$$E = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 \pm M I_1 I_2$$

Energy density of magnetic field

For ideal solenoid:



$$L = \mu n^2 V \qquad I = \frac{B}{\mu n}$$

$$W_m = \frac{1}{2} LI^2 = \frac{1}{2} \mu n^2 V \left(\frac{B}{\mu n} \right)^2 = \frac{1}{2} \frac{B^2}{\mu} V$$

$$w_m = \frac{W_m}{V} = \frac{1}{2} \frac{B^2}{\mu} = \frac{1}{2} \mu H^2$$

Example: coaxial cable shown below carries a current of I , Find the energy stored by a segment of the cable with length L .

solution:

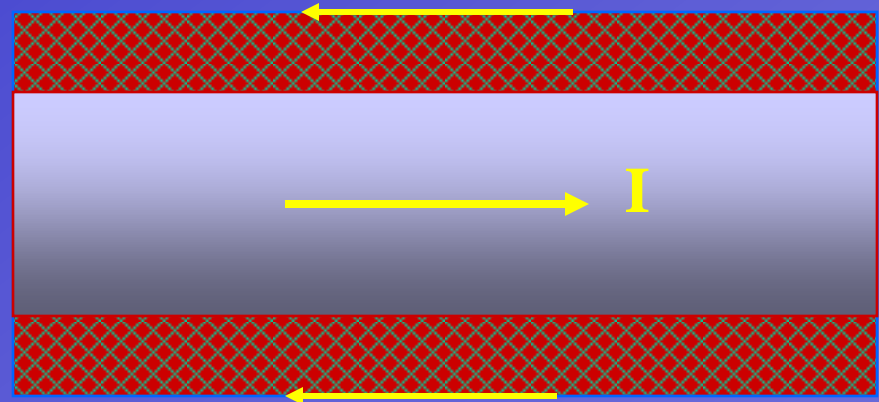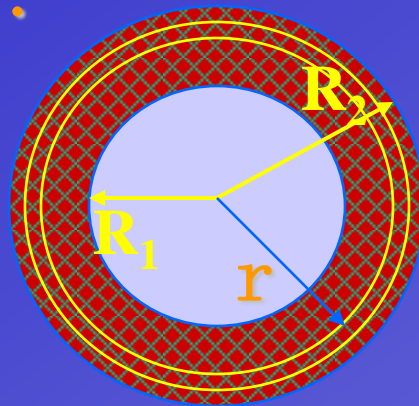

$$B = \frac{\mu_o I}{2\pi r} \quad w_m = \frac{B^2}{2\mu_o} = \frac{\mu_o I^2}{8\pi^2 r^2} \quad dV = 2\pi r l dr$$

$$W_m = \int_V w_m dV = \int_{R_1}^{R_2} \frac{\mu_o I^2}{8\pi^2 r^2} \cdot 2\pi l r dr$$

$$= \frac{\mu_o I^2 l}{4\pi} \int_{R_1}^{R_2} \frac{dr}{r} = \frac{\mu_o I^2 l}{4\pi} \ln \frac{R_2}{R_1}$$


Oscillation in circuit

If $E=0$, but loop
rule

$$L \frac{dI}{dt} + IR + \frac{Q}{C} = 0$$

Since: $I = \frac{dQ}{dt}$
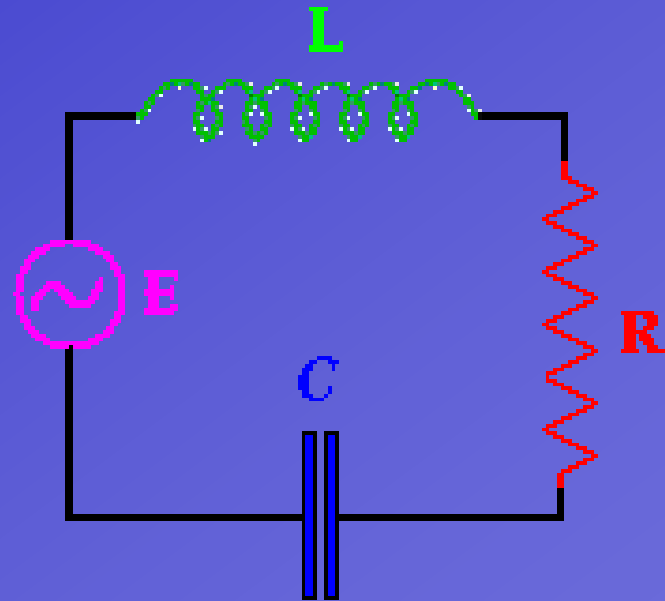
$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0$$



Compare with damped oscillation:

$$m \frac{d^2x}{dt^2} + f \frac{dx}{dt} + kx = \mathcal{E}$$

We have the angular frequency of RLC:

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

RLC circuit with AC source

Like forced oscillation:

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = V \sin \omega t$$

If R is small, and $\omega = \omega_0$

The magnitude of current has its maximum value, which is called electromagnetic resonance



Capacitive circuit




$$V_0 \sin \omega t = \frac{Q}{C}$$

$$I = \frac{dQ}{dt} = \omega C V_0 \cos \omega t$$

$$= \omega C V_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$

Capacitive reactance

$$X_c = \frac{1}{\omega C}$$

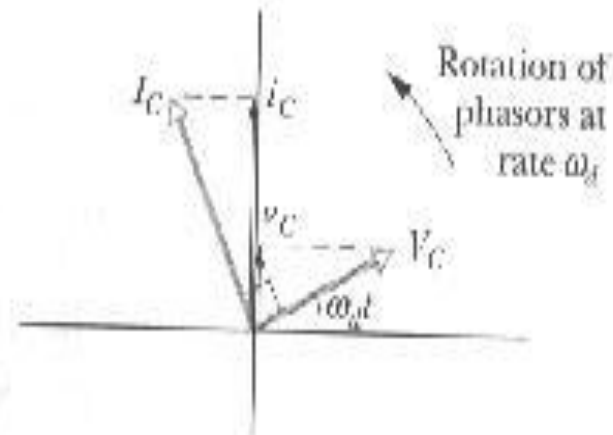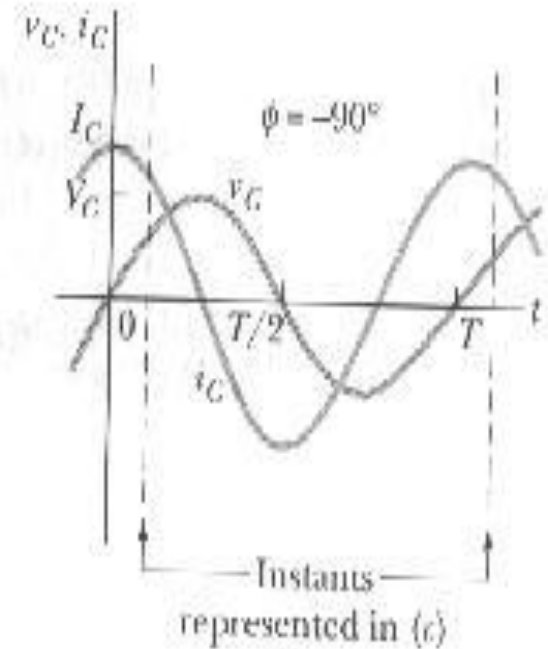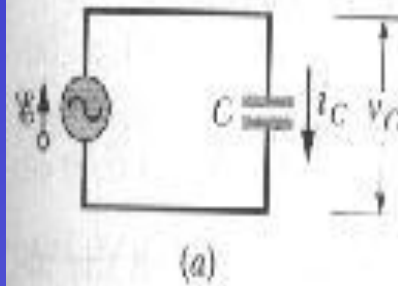


Inductive circuit

$$V_0 \sin \omega t = L \frac{dI}{dt}$$

$$I = -\frac{V_0}{\omega L} \cos \omega t$$
$$= \frac{V_0}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right)$$

Inductive reactance

$$X_L = \omega L$$

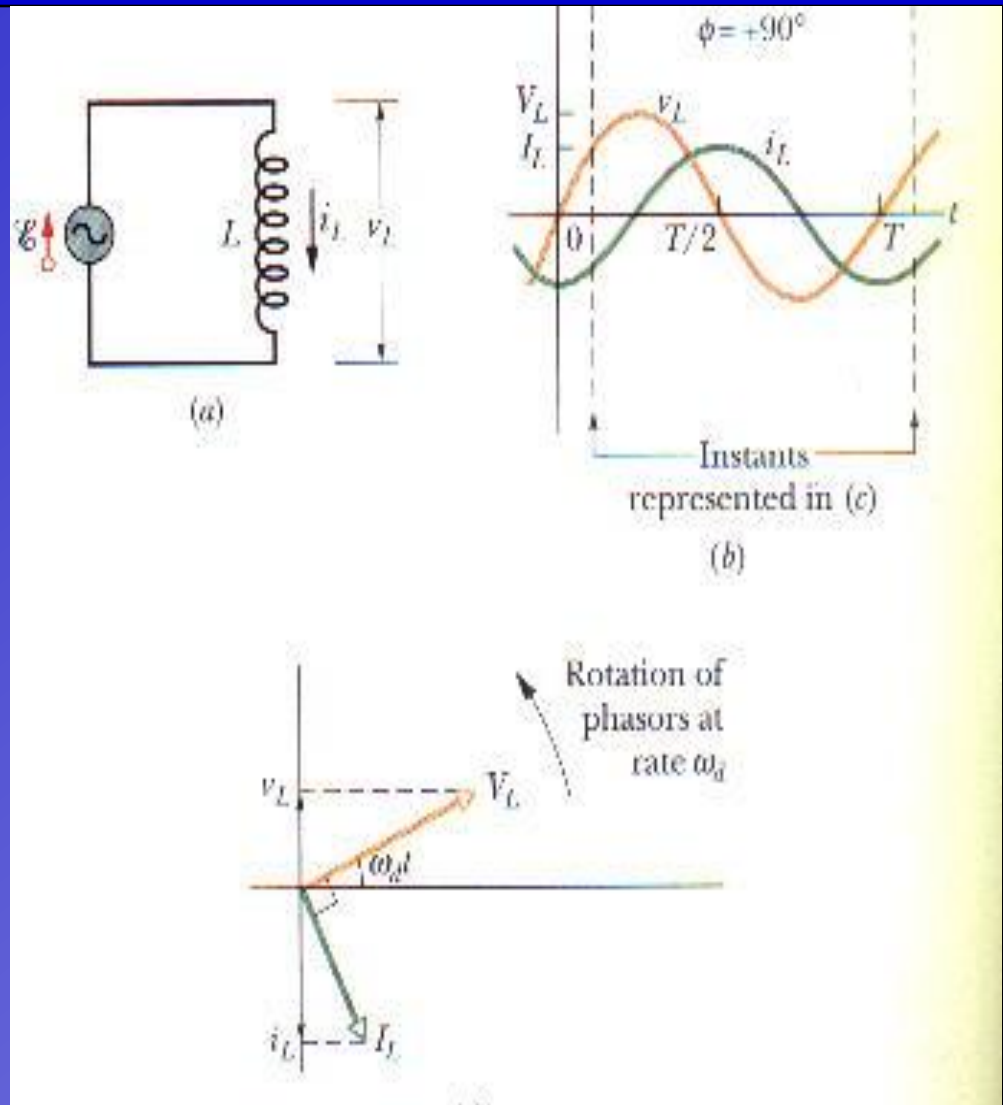

Impedance (电抗)

For RLC in series

$$Z = R + i(X_L - X_C)$$

$X_L > X_C$ the circuit is inductive

$X_L < X_C$ the circuit is capacitive

For RLC in parallel

$$\frac{1}{Z_{eff}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots$$

Phasor



where

$$\operatorname{tg} \varphi_0 = \frac{X_L - X_C}{R}$$

Ohm's Law in complex form

$$V = IZ$$

Example: The series RLC circuit is driven with an AC source of emf of the form of $V = V_0 \sin \omega t$

where $V_0 = 110 \text{ V}$, $f = 60 \text{ Hz}$, $R = 20.0 \Omega$, $C = 50.0 \mu\text{C}$,

$L = 5.00 \times 10^{-2} \text{ H}$, find the potential drops across the inductor, when V reach its maximum value.

Solution:

$$X_L = \omega L = 2\pi f L = 18 \Omega$$

$$X_C = \frac{1}{\omega C} = 53 \Omega$$

$$Z = 20 + j34 \Omega = 39 \angle -59^\circ \Omega$$

$$V_L = V_m \sin(\omega t - \frac{\pi}{2})$$

$$I = \frac{V}{Z} = \frac{110 \angle 90^\circ}{30 \angle -50^\circ} = 28 \angle -30^\circ \text{ A}$$

$$V_L = 28 \sin(\omega t - 30^\circ)$$

When V reaches its maximum value

$$\omega t = \frac{\pi}{2}$$